

CSE 3203 CT 4 Assignment

Roll No: 1903099

Instruction: Covert this doc to PDF while uploading.

Assignment Problem:

Build CPU based on following requirements:

1. Word Size of CPU = 5
2. ALU Operations = OR, ADD, ROL (2 bit)
3. Register Number = 4
4. Size of RAM = 7
5. Word size of ISA and RAM = 15 (7x15)
6. CPU Instructions = Register, Immediate, JMP, JNC

Solution:

[https://youtu.be/ UUmT5XhKJ4](https://youtu.be/UUmT5XhKJ4)


Simulator Design:

1. ALU Circuit (Show all circuits except FA circuit)(Marks 5):


Check List:

Have you added all circuits of ALU from FA to ALU Operations Circuits (ADD, XOR, SHL etc.) to Top Level ALU Circuit?	YES


5 bit Adder:

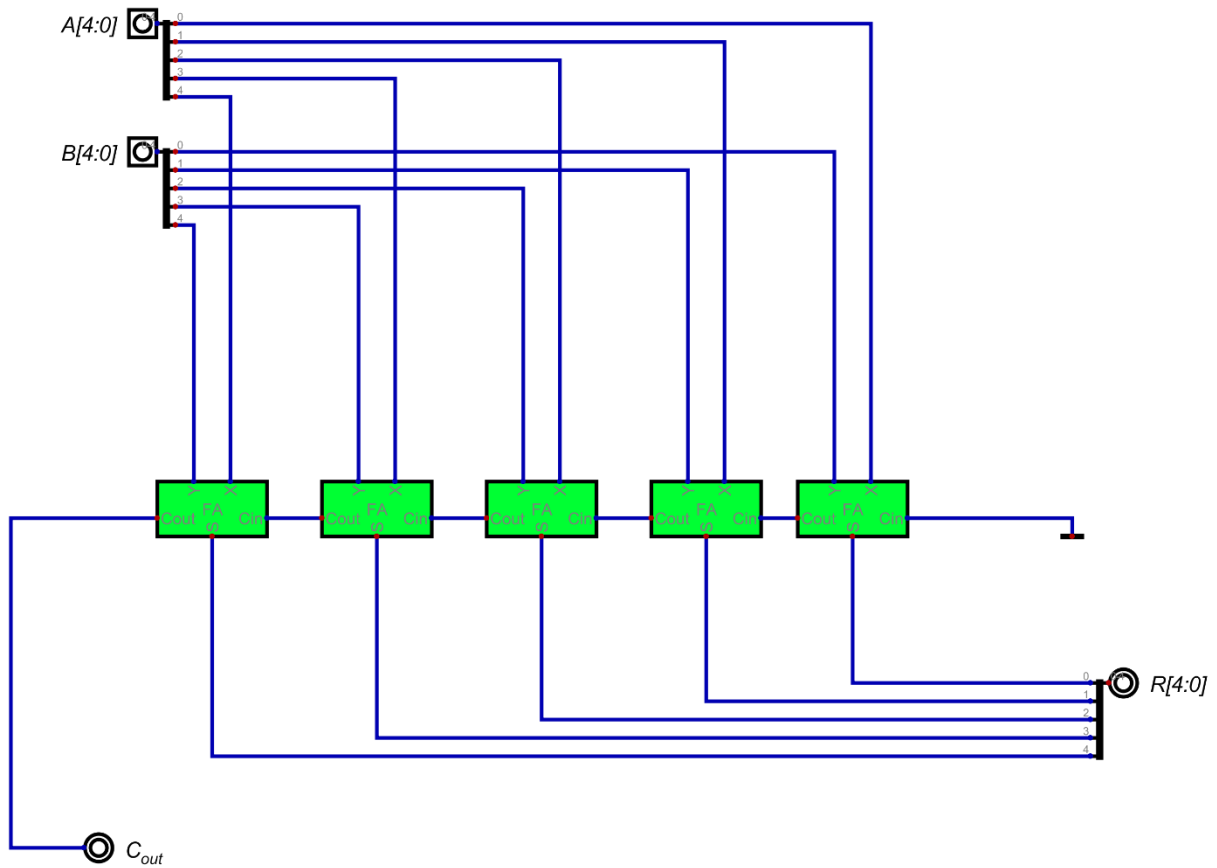


5 bit OR:

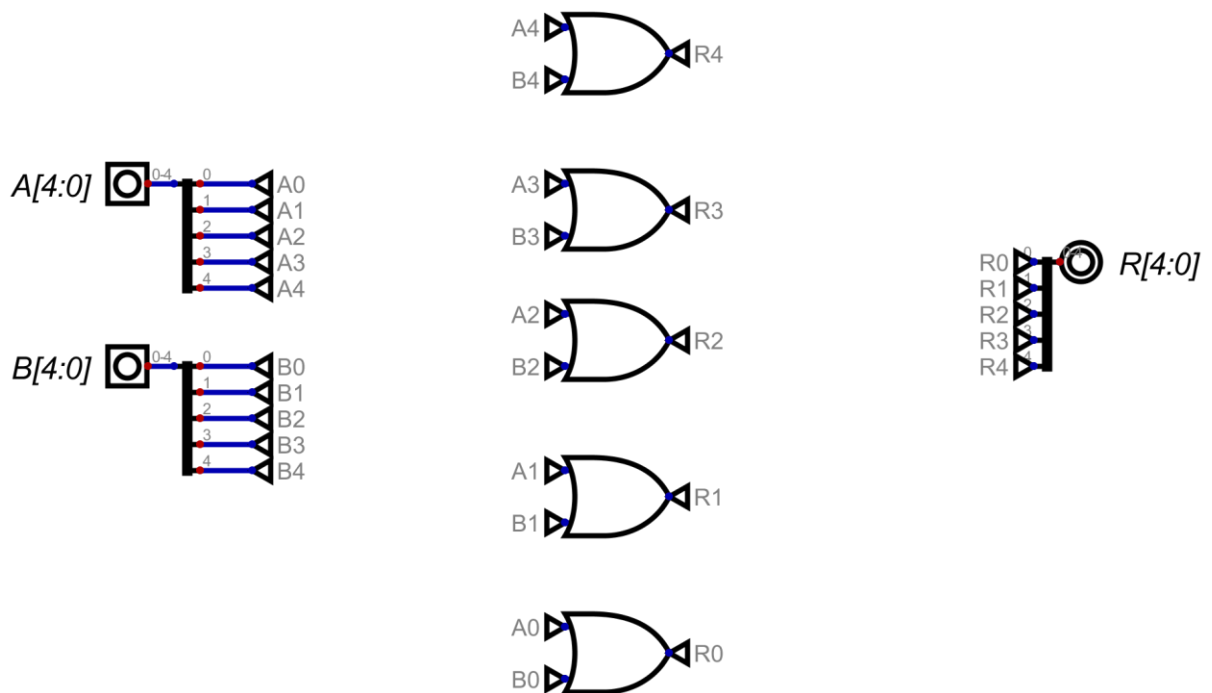

5 bit ROL:

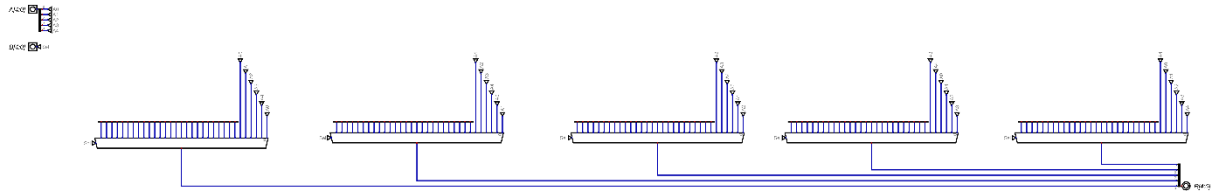

5 bit ALU:

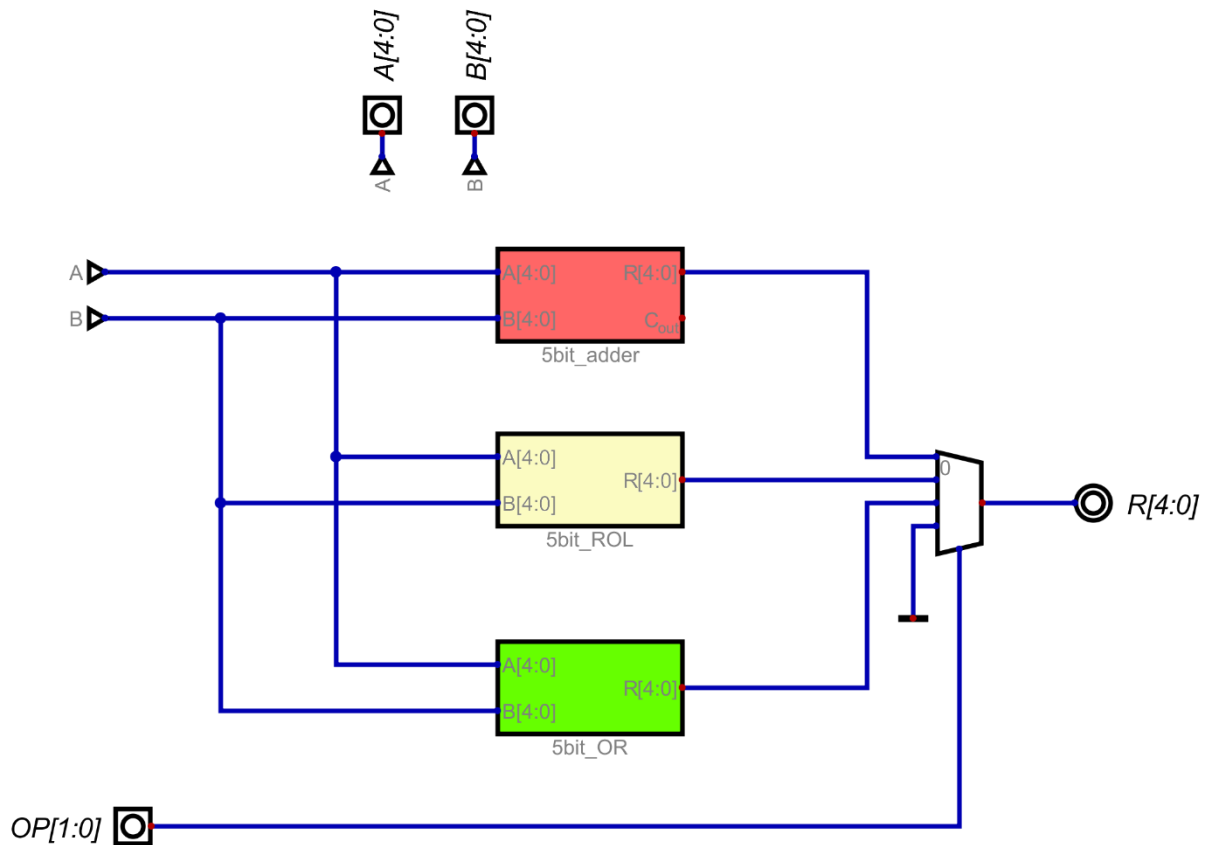


2. Register Set Circuit (Top to Bottom all circuits)(5 Marks):


Check List:

Have you added all circuits of Register Set from 1 bit Register to n bit Register to Top Level Register Set Circuit.?	YES


1 bit Register:

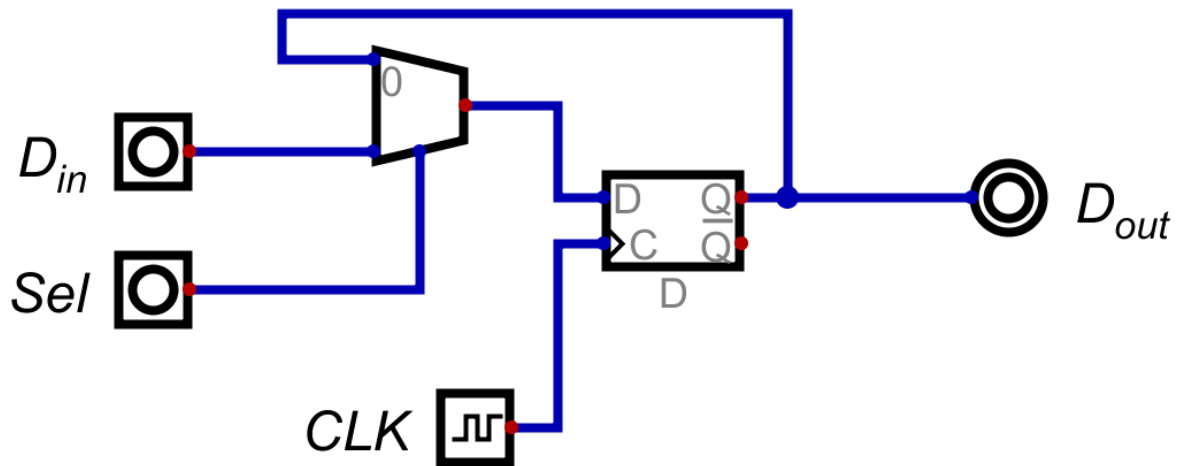

5 bit register:

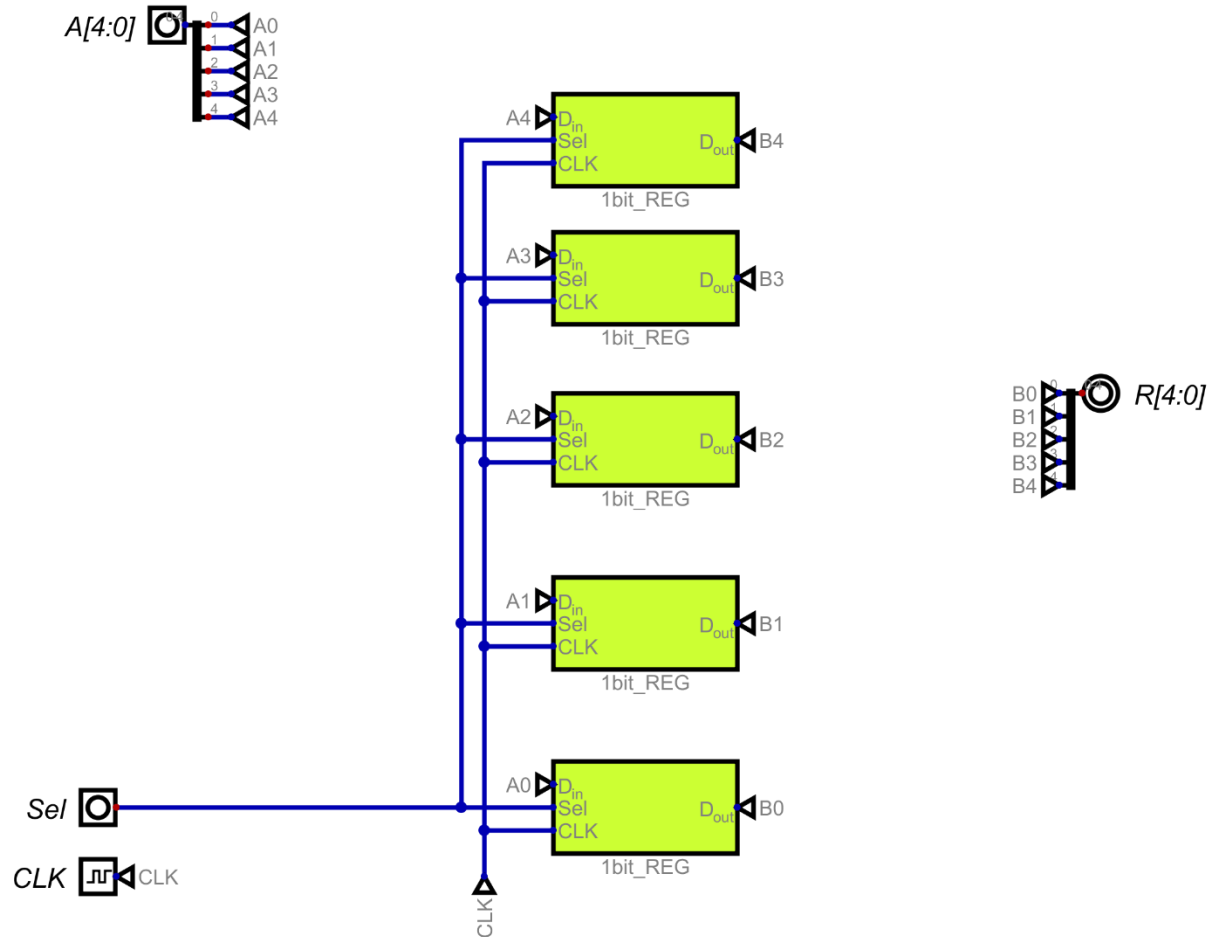

5 bit Register Set:

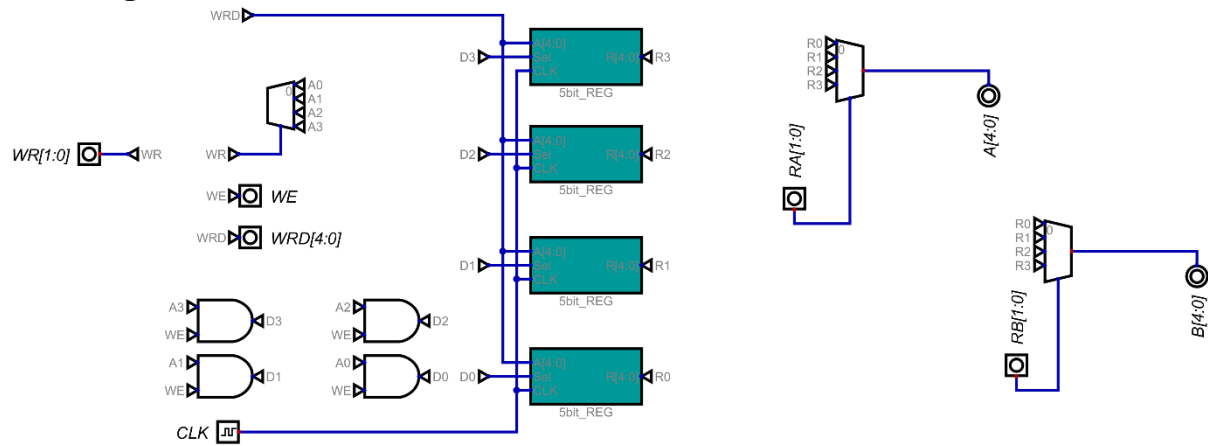


3. RAM Circuit (Top to Bottom all circuits)(5 Marks):


Check List:

Have you added all circuits of RAM from 1x1 RAM to 1xN RAM to MxN RAM?	YES


1x1 SRAM:

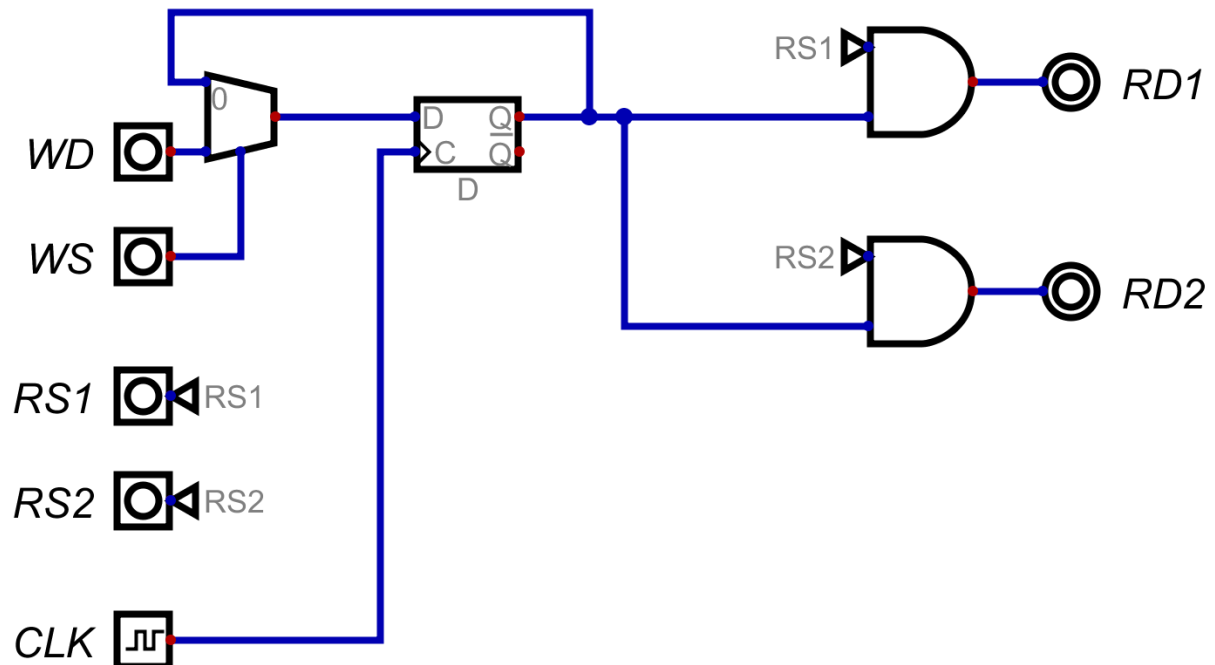

1x 15 SRAM:

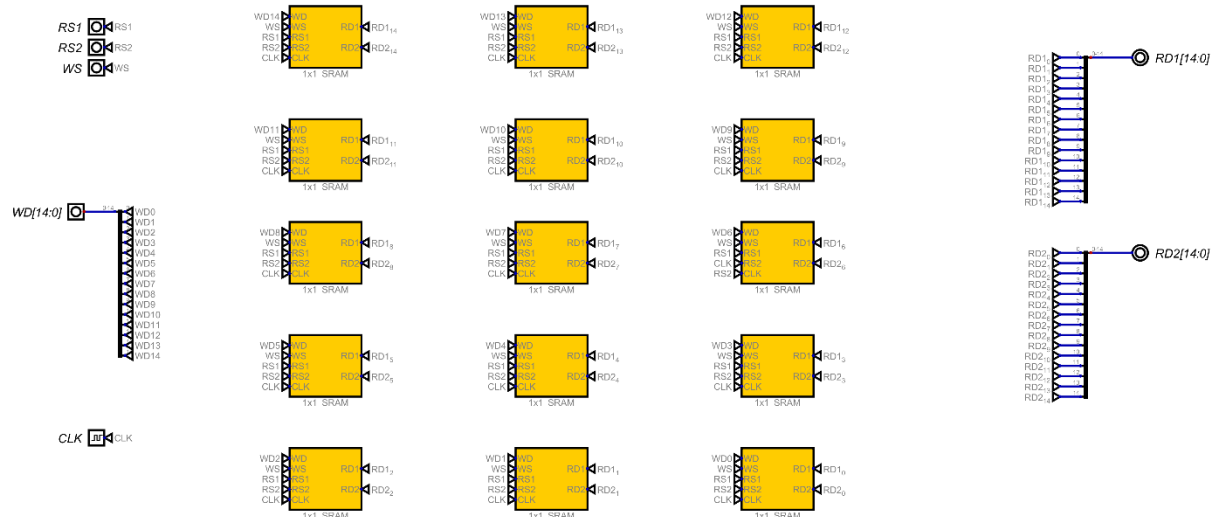

7x15 SRAM:

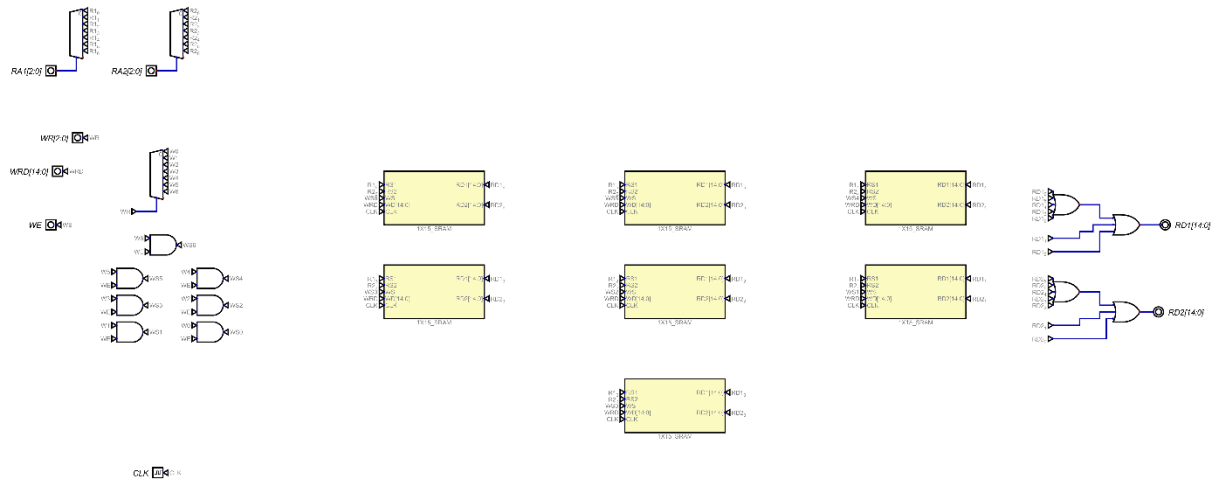

4. a) ISA (2 Marks)

Check List:

Have you added all ISA of CPU along with its sample machine code to be run on CPU?

YES/

ISA (Register Mode):

Opcode (6 bit)		Register 1	Register 2	Unused
2 bits	2 bits	2 bits	2 bits	7 bit
Types of instruction	Operations (ALU selection lines)	Ra (00-11)	Rb (00-11)	X

ISA (Immediate Mode):

Opcode (6 bit)		Register 1	value	Unused
2 bits	2 bits	2 bits	5 bit	4 bit
Types of instruction	Operations (ALU selection lines)	Ra (00-11)	Val(00000-11111)	X

Sample Machine Code with assembly code in comments to be run on CPU (You will make a video running this machine code on CPU in order to prove that your CPU is working perfectly)

Machine Code	Assembly Code
1001000100000000 0010010100000000 010001010010100	JE START START: OR R1,R1 JMP_TO: ADD R1,5

b) CPU (Top to Bottom all circuits)(3 Marks):


Check List:

Have you added all circuits of CPU from Program Counter to Control Unit to Top Level CPU Circuit with Output Pins showing contents of ALU, Register Set, RAM etc. (Important for CPU Verification, Check Tutorial Videos for Details)?	YES
Have you made a video running this sample machine code on the CPU (1 instruction at a time in a similar way shown in video) in order to prove that your CPU is working perfectly.	YES




Program Counter:

in  $I[2:0]$

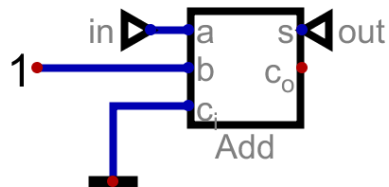


$O[2:0]$  out

PC Adder:

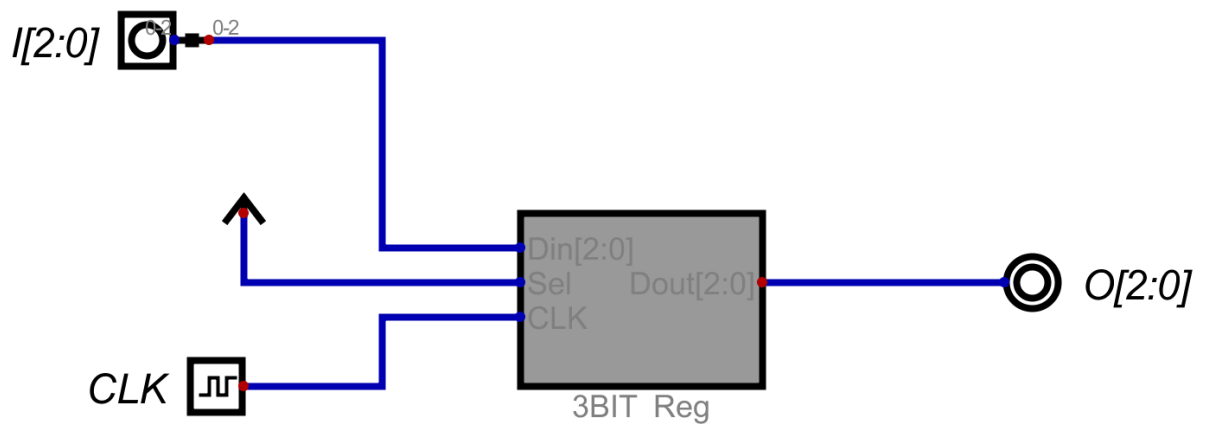

5bit Control Unit:

5 Bit Control Unit:

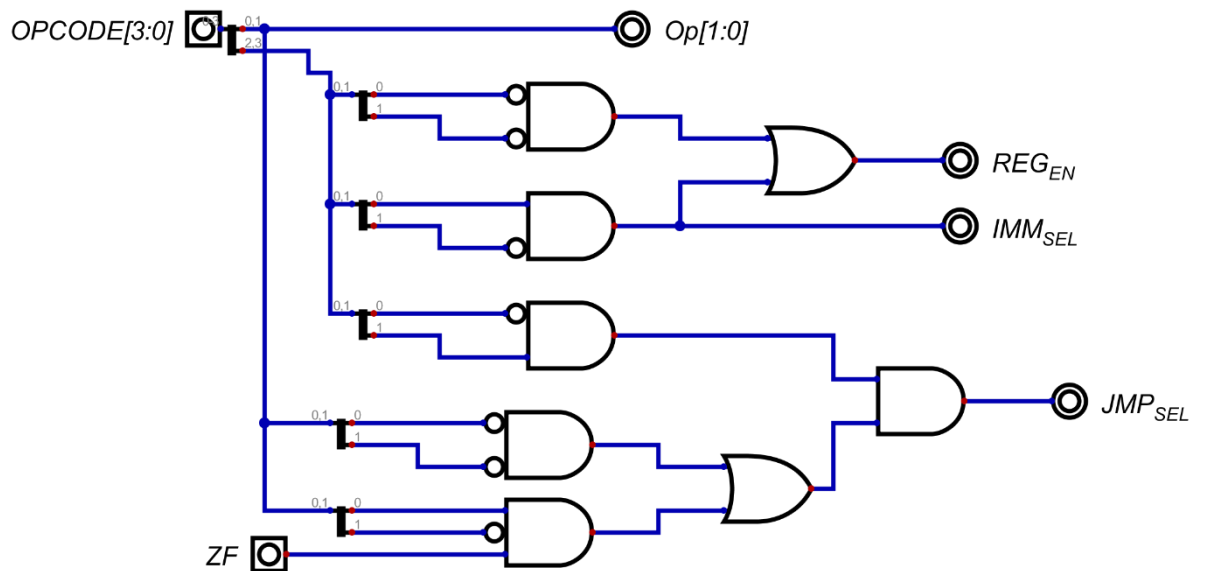

Main CPU:

Register Mode(00) = 2bit (type of operation) + 2bit(op) + 2bit(reg1) + 2bit(reg) + 7bit (don't Care)
 Immediate Mode(01) = 2bit (type of operation) + 2bit(op) + 2bit(reg1) + 5bit(value) + 4 bit(don't care)
 jump Mode(10) = 2bit (type of operation) + 2bit(op) + 4bit(add) + 7 bit(don't care)
 JMP(OP-00), JNC(OP-01)
 Op(00) = ADD
 Op(01) = ROL
 Op(10) = OR

JE START -> 1001000100000
 START: OR R1,R1 -> 001001010000000
 JMP_{TO}: ADD R1,5 -> 010001010010100
 JMP JMP_{TO} -> 1000000100000

